

## Homework set 5

(These problems should be done individually, not with project partner)

Due – As indicated on Canvas

### Instructions for submission

1) All answers are to be submitted in a **single** word/pdf file. This will be considered as a final submission.

\* **Submit only one pdf/docx for the complete homework.**

2) Include Quartus Prime, Modelsim and observation screenshots whenever possible with appropriate annotations for better presentation in word/pdf file.

**\*\*Do not submit extra screenshots in submission folder**

**\*\* Screen shots outside this pdf will not be graded**

3) Naming convention and files required

a) LastName\_FirstName\_HWSetI.docx/pdf - for Observations and Answers

b) **<Codefilename>.vhd/.v - coded by you, submit separately for each question outside the zip folder or paste in pdf/docx**

*\*Commenting of code, references and presentation of material also carries weight*

*\*You can add snippets of code if you want to show critical code*

### Important Instructions

**\*\*\*\*Start Early\*\*\*\***

\*\*\*\*Provide only Modelsim simulation and RTL view screenshots when mentioned in grading rubric

\*\*\*\*

1. **Synchronizer: Create an asynchronous data source and data sink using your favorite HDL.**
  - a. For the data source, create an Aclk of 50 MHz and use a toggle D flip-flop to generate the data. For the data sink, create a Bclk of 27.7 MHz and use a **3 Flip-Flop synchronizer** to read the data source.
    - i. Build this circuit in a SmartFusion2 device.
    - ii. Run a post-fit simulation in Modelsim for at least 20 clock cycles. Capture the screenshot.
    - iii. Run Smart Time and report any errors listed.
    - iv. Add a clock domain constraint to Smart Time to improve slack time. (Consider using a false path constraint to remove timing analysis in the path in the first synchronizer FF, or other timing constraints). Take a screenshot of the report after your constraints are applied.
    - v. What is the initial and resulting slack time?
  - b. Repeat (a) with an Aclk of 27.7 MHz, and a Bclk of 50 MHz.

Use this entity/module:

entity CDC3FF is

port (

Aclk : in std\_logic;

Bclk : in std\_logic;

```

    reset : in std_logic;
    Dout : out std_logic
);
end CDC3FF;

```

## 2. Going fast and slow.

- a. For the data source, create a 4-bit shift register in your favorite HDL language, fed by a toggle D flip-flop with a 100 MHz Aclk driving it. Use the 4-bits of the shift register as a parallel output. For the data sink, use a 4-bit input register driven by a 3.33 MHz clock. Use the SyncSignal method to synchronize the data coming in. Create the SyncSignal by using the slow clock as a data input to a FF clocked by the fast clock.
  - i. Place and route this circuit in the SmartFusion2 device. Determine the fMax. Run a post-fit simulation in Modelsim for at least 5 data transfers, be sure to capture a screenshot.
  - ii. How many data transfers are correct, with the intended data? If you add constraints can you improve the performance?
- b. Repeat (a) with the Aclk at 3.33 MHz, and the Bclk at 100 MHz.

*\*\* you may need to have two different codes for Question 2, one for a and the other for b.*

Use this entity/module:

```

entity SlowFast is
port (
    Aclk, Bclk : in std_logic;
    reset : in std_logic;
    Dout : out std_logic_vector(3 downto 0)
);
end SlowFast;

```

## Grading Rubric

### 1) - [10 points]

[5 point] Implementation Verilog/VHDL Code

[5 point] Simulation Screenshots (Modelsim), RTL view screen-shot, Observations

### 2) - [10 points]

[5 point] Implementation Verilog/VHDL Code - Two separate code

[3 point] Simulation Screenshots (Modelsim),

[2 point] Observations, RTL view screenshot